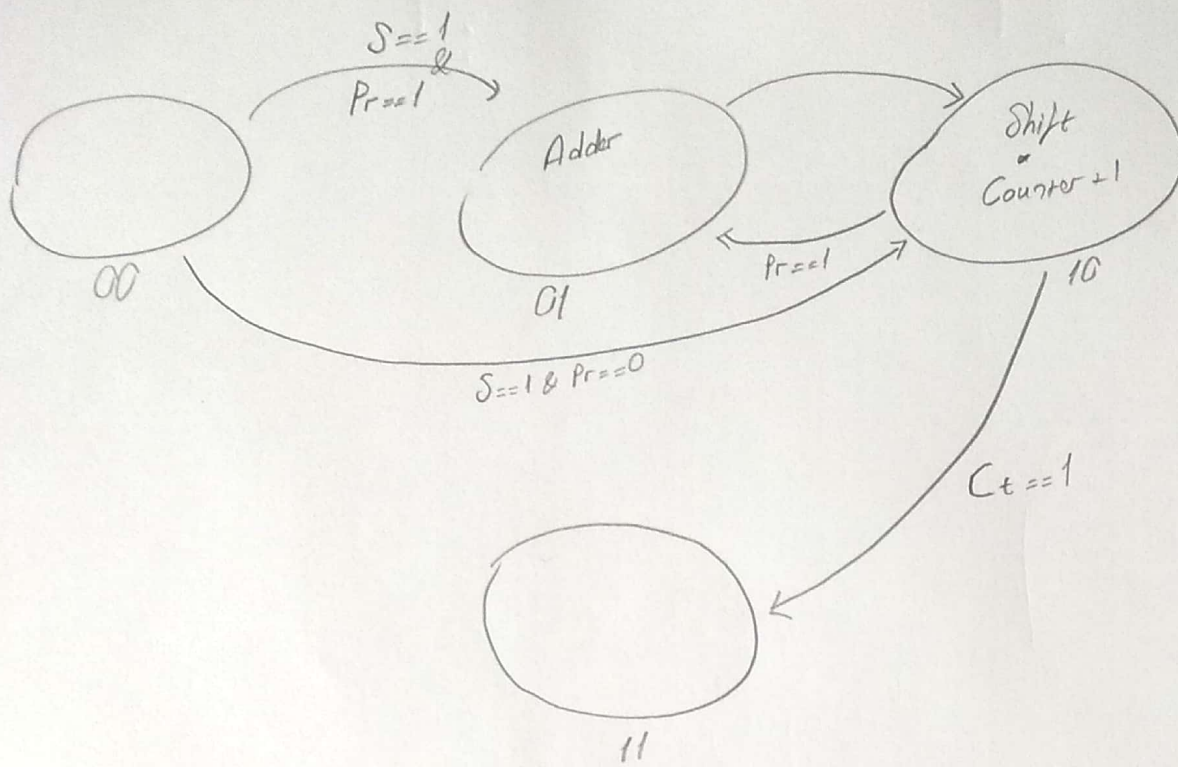


- ✚ I designed my adder and shifter for extra point.
- ✚ My design work correctly all situation.
- ✚ Program will start when you write 1 bit to start bit. Program doesn't have restart buton. You have to reset program.

DataPath

- ❖ I used one adder and one shifter. Adder and shifter has enable bit. Example, When adder enable bit come, adder will work.
- ❖ Counter will work when CT signal is one. Counter will work until 32.
- ❖ I used two mux.
 - Upper mux that chose first multiplier when counter 0, after that mux choose shifter RESULT-R.
 - Down mux that choose the adder result or shifter result. Because sometimes adder doesn't work so if this be,mux choose shifter result.



S_1	S_0	S	Pr	Ct	N_1	N_0	Addr	Sh	C	
0	0	0	x	x	0	0	0	0	0	$N_1 = S_1' S_0' Pr' S + S_1' S_0 + S_1 S_0' Pr' Ct' + S_1 S_0' Ct$
0	0	1	0	x	1	0	0	1	1	$N_0 = S_1' S_0' S Pr + S_1 S_0' Pr Ct' + S_1 S_0' Ct + S_1 S_0$
0	0	1	1	x	0	1	1	0	0	$A = S_1' S_0' S Pr + S_1 S_0' Pr Ct'$
0	1	x	x	x	1	0	0	1	1	$Sh = S_1' S_0' S Pr' + S_1' S_0 + S_1 S_0' Pr' Ct'$
1	0	x	1	0	0	1	1	0	0	
1	0	x	0	0	1	0	0	1	1	
1	0	x	x	1	1	1	0	0	0	
1	1	x	x	x	1	1	0	0	0	

$S = \text{start}$

$Pr = \text{Product control}$

$Ct = \text{Counter equal to 22 or not}$

$C = \text{Counter enable signal}$

$Sh = \text{Shifter enable signal}$